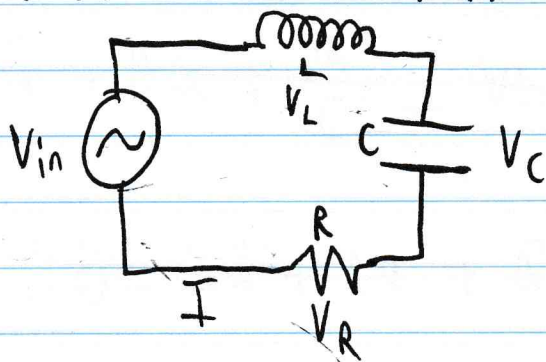


## Unit 2 Lesson 9

For an RLC circuit of the form



, where  $V_k$  is the voltage drop across  $k$ ; we have  
 $I$  is the current of the circuit,

$L$  is inductance

$R$  is resistance

$C$  is capacitance

$V_{in}$  is voltage input

$Q(t)$  is the charge on the capacitor, etc.

We have

$$V_L = L \dot{I}$$

$$V_C = Q/C$$

$$V_R = RI$$

We are given a few DEs extracted from this scenario:

$$\cancel{L\ddot{q} + R\dot{q} + \frac{q}{C} = V_{in}}$$

for

$$p(d) \equiv L\ddot{a} + R\dot{a} + \dot{a}^T q,$$

$$p(d) q = V_{in}$$

$$p(d) \dot{I} = \dot{V}_{in}$$

$$p(d) V_c = \frac{1}{C} \dot{V}_{in}$$

$$p(d) V_r = R \dot{V}_{in}$$

### Example Problem

By experimentation with the math let, it seems that capacitance in the range of 50  $\mu\text{f}$  puts inductance and  $V_o$  in phase.